




Module: R3: DLD + DSD**Section: Combination Circuits Task: Assignment 1****Assignment 1****Combination Circuits****1. 1's and 2's Complement:**■ **Solution:****2. 3-to-8 Line Decoder using 2-to-4 Decoders:**■ **Solution:**

Table for 3x8			
A	B	C	F
0	0	0	m0
0	0	1	m1
0	1	0	m2
0	1	1	m3
1	0	0	m4
1	0	1	m5
1	1	0	m6
1	1	1	m7

The block-level implementation will look following:



  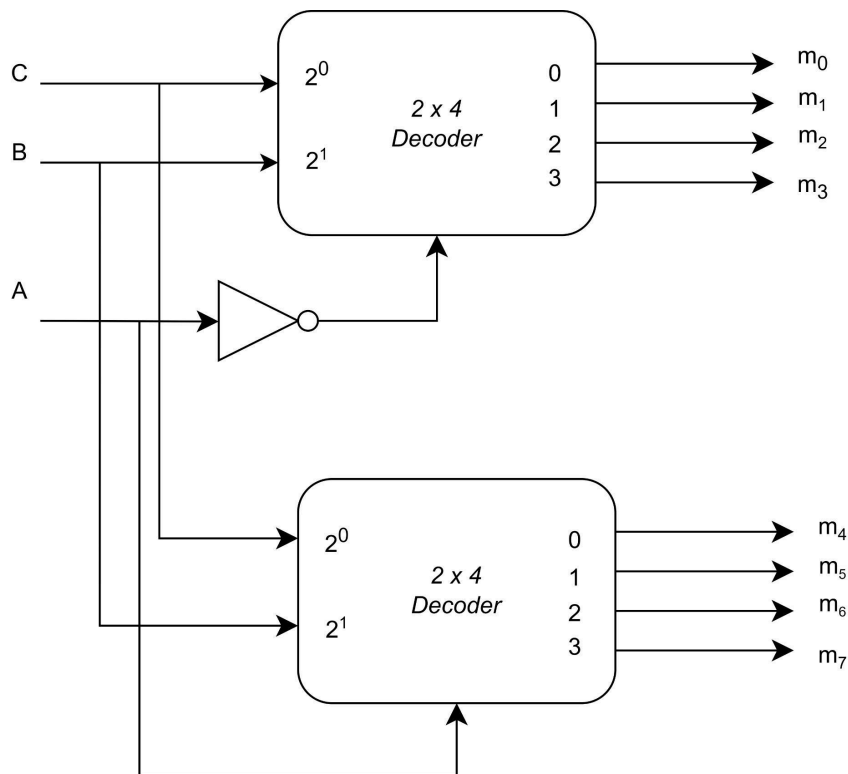
This decoder can be further broken down to two **2 x 4** decoders. The input A can be used to enable either of the two **2 x 4** decoders. The implementation is given below:



 3. Implement a full-adder with two 4 x 1 multiplexers:

■ Solution:


A full adder can be implemented using two 4 x 1 multiplexers, one for each of sum and carry. A block level implementation of the full adder is as follows:



The block can be further broken into two 4 x 1 multiplexers. Using truth tables:

Truth table for Sum				
Select Lines				
x	y	z	Sum	F
0	0	0	0	F = z
0	0	1	1	
0	1	0	1	F = z'
0	1	1	0	
1	0	0	1	F = z'
1	0	1	0	
1	1	0	0	F = z
1	1	1	1	


Truth table for Carry				
Select Lines				
x	y	z	Carry	F
0	0	0	0	F = 0
0	0	1	0	
0	1	0	0	F = z
0	1	1	1	
1	0	0	0	F = z
1	0	1	1	
1	1	0	1	F = 1
1	1	1	1	

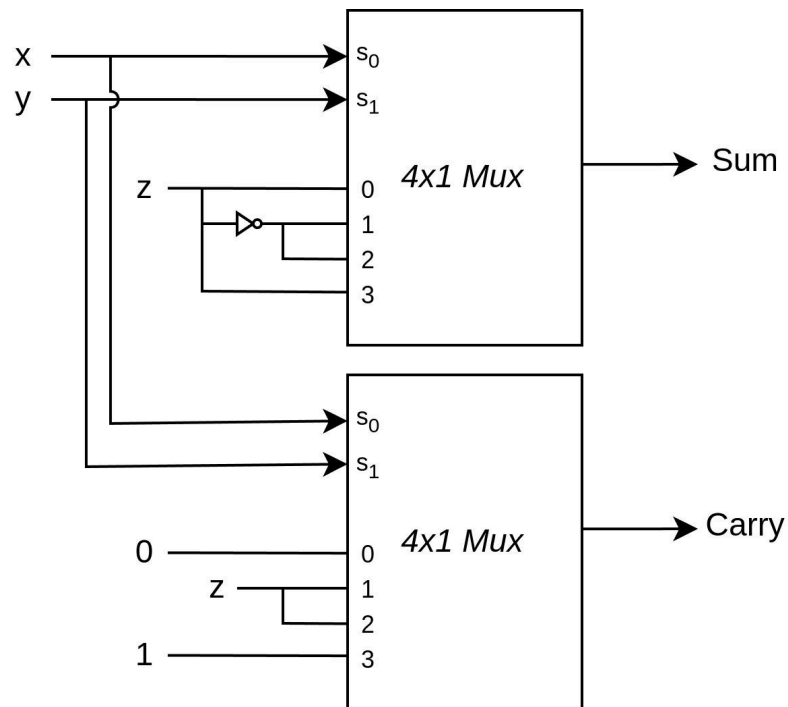

4. Implement $F = \sum m(1, 2, 3, 6, 7)$ using 4 x 1 mux:

■ Solution:

Truth table				
Select Lines				
A	B	C	$F = \sum m(1, 2, 3, 6, 7)$	F
0	0	0	0	F = C
0	0	1	1	
0	1	0	1	F = 1
0	1	1	1	
1	0	0	0	F = 0
1	0	1	0	
1	1	0	1	F = 1
1	1	1	1	

 


5. NOR circuit realization of the function $f = (b + c + d)(a' + b + c)(a' + d)$:

■ **Solution:**

Simplifying the function gives us the following equation for NOR equivalent circuit.

 
$$f = [(b+c+d)' + (a'+b+c)' + (a'+d)']'$$




6. BCD-to-excess-3-code converter:

■ **Solution:**


The block level implementation will look like the following. Here's we will be adding 3 (0011) to each bit of the BCD code to create an excess-3 code at output using a 4-bit adder circuit.

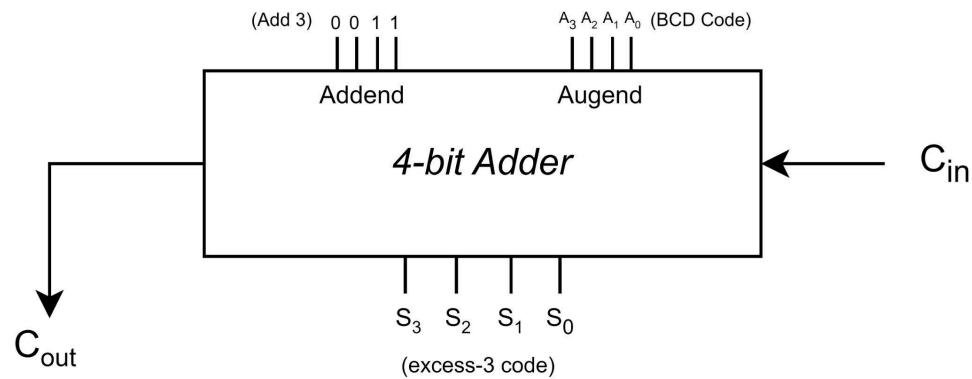

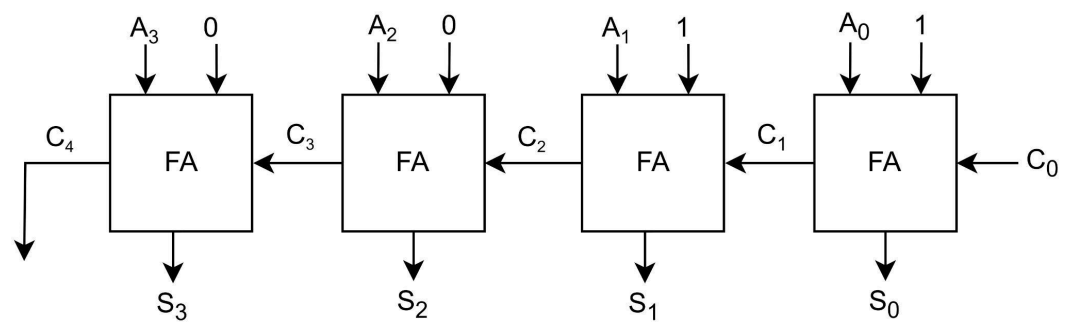The 4-bit Adder is further broken down into 4 full-adder circuits. This is illustrated in the following:




 C_0 in this case will be 0, since we are performing addition. In order to convert this circuit into excess-3-code-to-BCD converter, we will need to set C_0 to 1 and alter our logic using xor gates to perform subtraction (Excess-3 code) - 3 = (BCD code). The circuit will look like this:



7. 4-bit Input Parity Generator:

■ Diagram:

 

4-bit Even Parity Generator

■ Verilog Code:

```

module parity_generator ( input [3:0] data, output reg
parity);

always @*
begin
    assign parity = data[0] ^ data[1] ^ data[2] ^
data[3];
end
endmodule

```

■ Testbench:

```

`timescale 1ns/1ps
module test_tb;

    reg [3:0] data;
    wire parity;

    parity_generator dut(.data(data), .parity(parity));

    // Stimulus
    initial begin
        // Test with different inputs
        data = 4'b0000; // Even number of high bits
    end
endmodule

```

```

#20;
data = 4'b0001; // Odd number of high bits
#20;
data = 4'b1100; // Even number of high bits
#20;
data = 4'b1011; // Odd number of high bits
#20;
data = 4'b0000; // Even number of high bits
#20;
data = 4'b1101; // Odd number of high bits
#20;
end
endmodule

```

■ Output:

