 


**Module: R3: DLD + DSD****Section: Sequential Circuits Task: Assignment 2****Assignment 2**  
**Sequential Circuits****➤ Question 1: Design button press synchronizer:****a. FSM Diagram:****b. Truth Table:**

One-Hot Encoding	S0 = 001	S1 = 010	S2 = 100
------------------	----------	----------	----------

Present State			Input	Next State			Output	Inputs to Flip-Flops		
Q <sub>C</sub>	Q <sub>B</sub>	Q <sub>A</sub>	b <sub>i</sub>	Q <sub>C+1</sub>	Q <sub>B+1</sub>	Q <sub>A+1</sub>	b <sub>o</sub>	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	1	0	0	0	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	1	0	0	1	1	0	0
1	0	0	0	0	0	1	0	0	0	1
1	0	0	1	1	0	0	0	1	0	0

### c. Circuit Diagram:

Using K-Maps:

$Q_C Q_B$		$Q_A b_i$				$Q_B$
		00	01	11	10	
$Q_C$	00	X	X	0	0	$Q_B$
	01	1	1	X	X	
	11	X	X	X	X	
	10	0	X	X	X	
		$b_i$				

$b_o = Q_B$

$Q_C Q_B$		$Q_A b_i$				$Q_B$
		00	01	11	10	
$Q_C$	00	X	X	0	1	$Q_B$
	01	0	0	X	X	
	11	X	X	X	X	
	10	1	0	X	X	
		$b_i$				

$D_A = Q_B' b_i'$


$Q_C Q_B$		$Q_A b_i$				$Q_B$
		00	01	11	10	
$Q_C$	00	X	X	1	0	$Q_B$
	01	0	0	X	X	
	11	X	X	X	X	
	10	0	0	X	X	
		$b_i$				

$D_B = Q_A b_i$

$Q_C Q_B$		$Q_A b_i$				$Q_B$
		00	01	11	10	
$Q_C$	00	X	X	0	0	$Q_B$
	01	1	1	X	X	
	11	X	X	X	X	
	10	0	1	X	X	
		$b_i$				

$D_C = Q_B Q_A' + Q_C b_i$

Here's the final circuit:

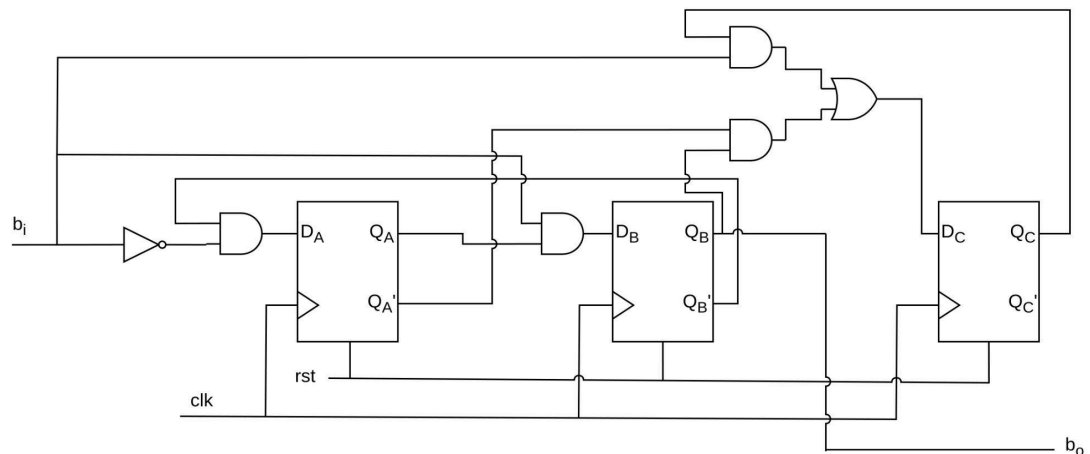

**d. Verilog Code:**

```

    module button_press_synchronizer (input clk, rst, bi,
output reg bo);

    localparam S0 = 3'b001;
    localparam S1 = 3'b010;
    localparam S2 = 3'b100;

    reg [2:0] state;

    always @(posedge clk or posedge rst)
    begin
        if (rst)
            state <= S0;
        else
            begin
                case (state)
                    S0 : state <= bi? S1 : S0;

                    S1 : state <= S2;

                    S2 : state <= bi ? S2 : S0;
                endcase
            end
        end

    always @(state)
        case (state)
            S0 : bo <= 0;

            S1 : bo <= 1;

            S2 : bo <= 0;

            default : bo <= bo;
        endcase
    endmodule

```

**e. Testbench:**

```
module tb_button_press_synchronizer;
    reg clk, rst, bi;
    wire bo;

    button_press_synchronizer m1 (.clk(clk), .rst(rst), .bi(bi),
    .bo(bo));

    always #5 clk = ~clk;
    initial begin

        $dumpvars;

        clk = 0;
        rst = 0;
        bi = 0;

        #10;
        rst = 1;
        bi = 1;

        #20
        rst = 0;

        #30;
        bi = 0;

        #20;
        bi = 1;

        #50;
        bi = 0;

        #10;
        bi = 1;


        #20;
        bi = 0;

        $finish;
    end
endmodule
```

```
end
```


```
endmodule
```

### f. Output:

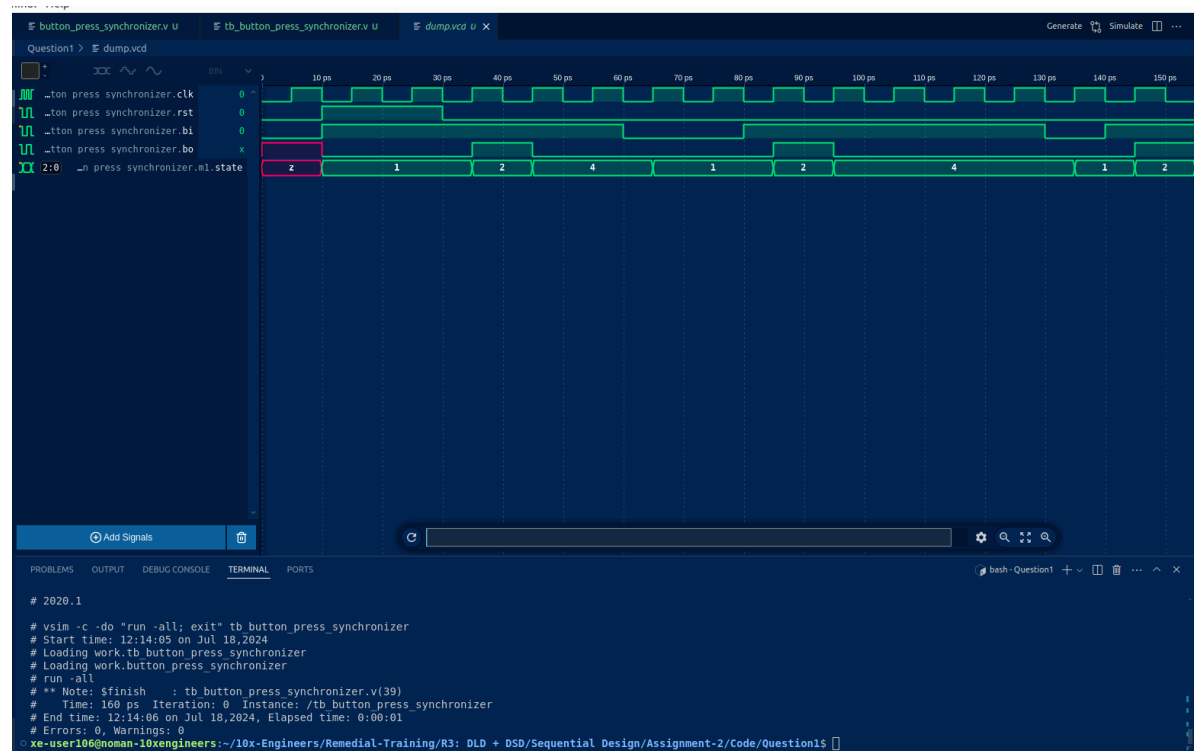

### ➤ Question 2: Serial Input 2's Complementer:


g. State Diagram:

 


**h. State Table:**

Present State	Input	Next State	Output	Flip-Flop Input
$Q_t$	$x$	$Q(t+1)$	$y$	$D$
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	0	1


K-maps:

 


$$D = x + A$$

 

$$y = x \oplus A$$

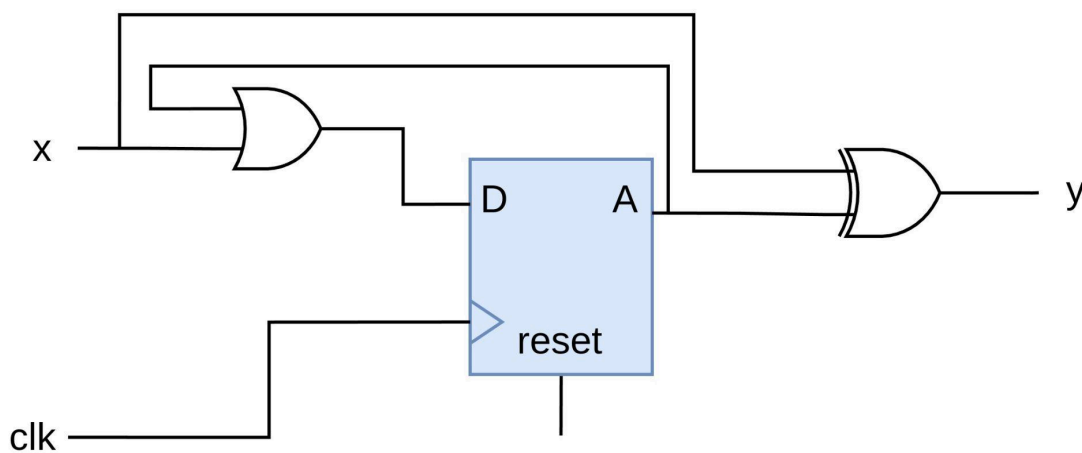
**i. Circuit Diagram:**

➤ **Question 3: Timing Diagram:**

 





➤ **Question 4: Pulse Detector:**

a. **FSM Diagram:**

 


**b. Truth Table:**

One-Hot Encoding				A = 001		B = 010		C = 100		
Present State			Input	Next State			Output	Inputs to Flip-Flops		
Q <sub>C</sub>	Q <sub>B</sub>	Q <sub>A</sub>	x	Q <sub>C+1</sub>	Q <sub>B+1</sub>	Q <sub>A+1</sub>	y	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	1	0	0	0	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	1	0	1	0
1	0	0	0	0	0	1	0	0	0	1
1	0	0	1	0	0	1	0	0	0	1

    **c. Circuit Diagram:**



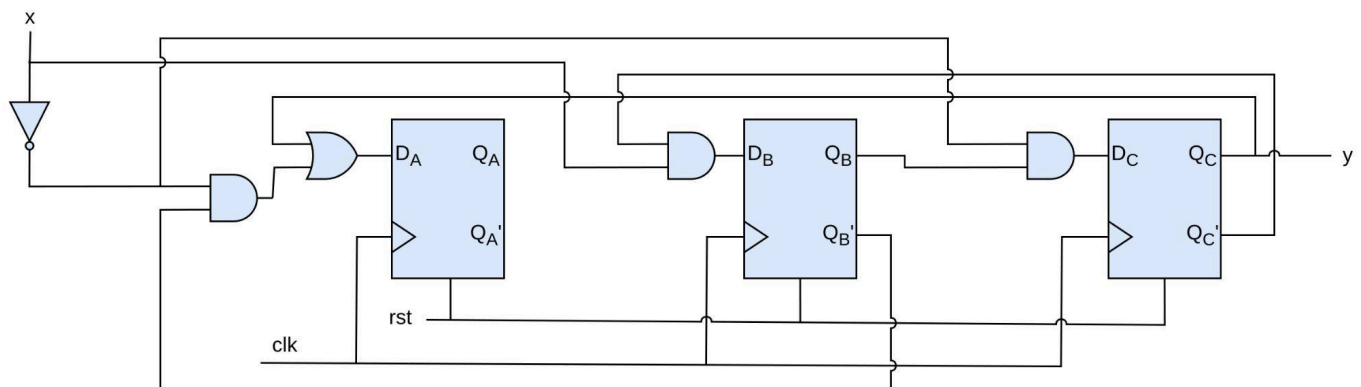

#### d. Verilog Code:

```
module pulse_detector (input clk, rst, x, output reg y);
```

```
    localparam A = 3'b001;
```

```
    localparam B = 3'b010;
```

```
    localparam C = 3'b100;
```

```
    reg [2:0] state, next_state;
```

```
    reg x_previous;
```

```
    //State-Transition
```

```
    always @(posedge clk or rst)
```

```
    begin
```

```
        if (rst)
```

```
            state <= A;
```

```
        else
```

```
            state <= next_state;
```

```
    end
```

```
    //Next-State Logic
```

```
    always @(*)
```

```
    begin
```

```
        case (state)
```

```
            A :
```

```
            begin
```

```
                if (!x)
```

```
                    next_state <= A;
```

```

        else
            next_state <= B;
        end

    B :
    begin
        if (!x && x_previous)
            next_state <= C;
        else
            next_state <= B;
        end

    C : next_state <= A;
    default : next_state <= A;
    endcase
end

//Output
always @(posedge clk or posedge rst)
begin
    if (rst)
        y <= 0;
    else if (state == C)
        y <= 1;
    else
        y <= 0;
end

//Detect Falling-Edge
always @(posedge clk or posedge rst)
begin
    if (rst)
        x_previous <= 1;
    else
        x_previous <= x;
end

endmodule

```

**e. Testbench:**

```
module tb_pulse_detector;
```

```
reg clk, rst, x;
wire y;

pulse_detector m0 (.clk(clk), .rst(rst), .x(x), .y(y));

always #5 clk = ~clk;

initial begin
    $dumpvars;

    clk = 0;
    rst = 0;
    x = 1;
    #20;

    rst = 1;
    #20;

    rst = 0;
    #10;

    x = 0;
    #20;

    x = 1;
    #20;

    x = 0;
    #30;

    x = 1;
    #40;

    rst = 1;
    #10;

    x = 0;
    #30;


    x = 1;
    rst = 0;
    #40;
```

```

$finish;
end
endmodule

```


### f. Output:

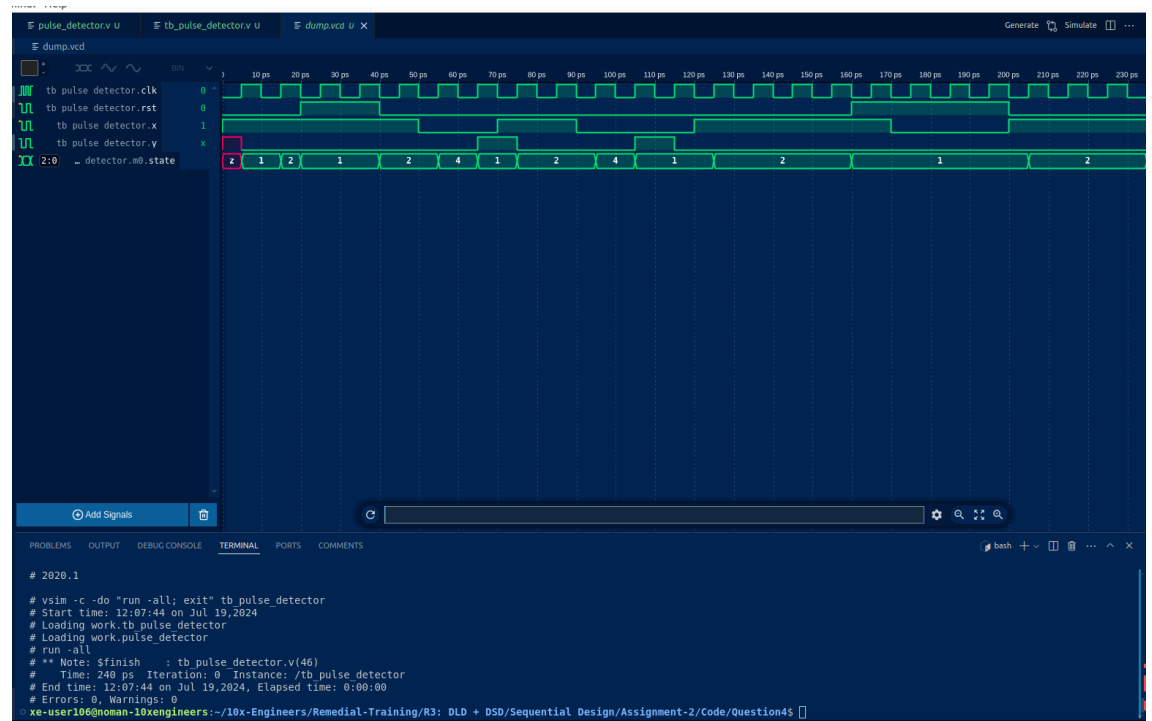

### ➤ Question 5: Asynchronous reset:

Since we are dealing with 2 different clock domains. Hence, in order to avoid any glitches or metastability, I'll be using a two-flop synchronizer circuit to map the **reset\_A** signal synchronously with clock of domain B (**clk\_B**)

#### a. Circuit Diagram:

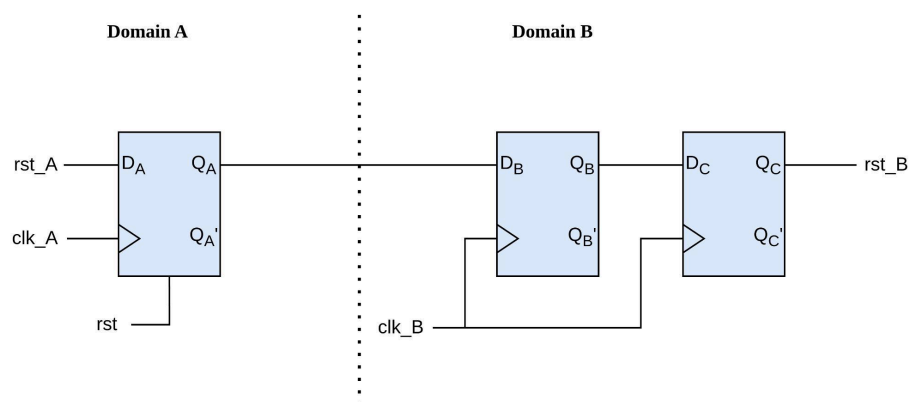

**b. Verilog Code:**

```

module d_ff (input clk, rst, d, output reg q);

always @(posedge clk or posedge rst) begin
    if (rst)
        q <= 1'b0;
    else
        q <= d;
end
endmodule

module synchronizer (input clk_A, clk_B, rst_A, rst, output
reg rst_B);

    wire w0, w1, w2;

    d_ff m0 (.clk(clk_A), .rst(rst), .d(rst_A), .q(w0));

    //Two Flops Synchronizer
    d_ff m1 (.clk(clk_B), .rst(1'b0), .d(w0), .q(w1));
    d_ff m2 (.clk(clk_B), .rst(1'b0), .d(w1), .q(w2));

    assign rst_B = w2;

endmodule

```

**c. Testbench:**

```

module tb_synchronizer;
    reg clk_A, clk_B, rst, rst_A;
    wire rst_B;

    synchronizer dut (.clk_A(clk_A), .clk_B(clk_B), .rst(rst),
.rst_A(rst_A), .rst_B(rst_B));

    always #5 clk_A = ~clk_A;
    always #20 clk_B = ~clk_B;

    initial begin

```

```
$dumpvars;

clk_A = 0;
clk_B = 0;
rst = 0;
rst_A = 0;

#20;

rst = 1;
#10;
rst_A = 1;
#40;

rst = 0;
#40;

rst_A = 0;
#80;

rst_A = 1;
#20;

rst_A = 0;
#30;

rst_A = 1;
#30;

rst_A = 0;
#100;

$finish;

end
endmodule
```

**d. Output:**

